

Міністерство освіти і науки України
Національний університет «Львівська політехніка»

Кафедра ЕОМ



Звіт

до лабораторної роботи № 3

з дисципліни «Моделювання комп'ютерних систем» на
тему:

«Поведінковий опис цифрового автомата Перевірка роботи автомата за
допомогою стенда Elbert V2 – Spartan 3A FPGA»

Варіант №18

Виконав:
ст. гр. КІ-201
Луцик Н. І.
Прийняв:
ст. викладач
каф. ЕОМ
Козак Н. Б.

Львів 2024

Мета роботи: На базі стенда реалізувати цифровий автомат для обчислення значення виразів.

Завдання:

ВАРІАНТ(KI-201)	ВИРАЗ
18	$((OP1 + OP2 + 10) * 2) \ll OP2$

Задані числа:

OP1= 0000 0001(2) = 1(10)

OP2= 0000 0010(2) = 2(10)

Результат = 0110 1000 (2) = 104(10)

Виконання завдання:

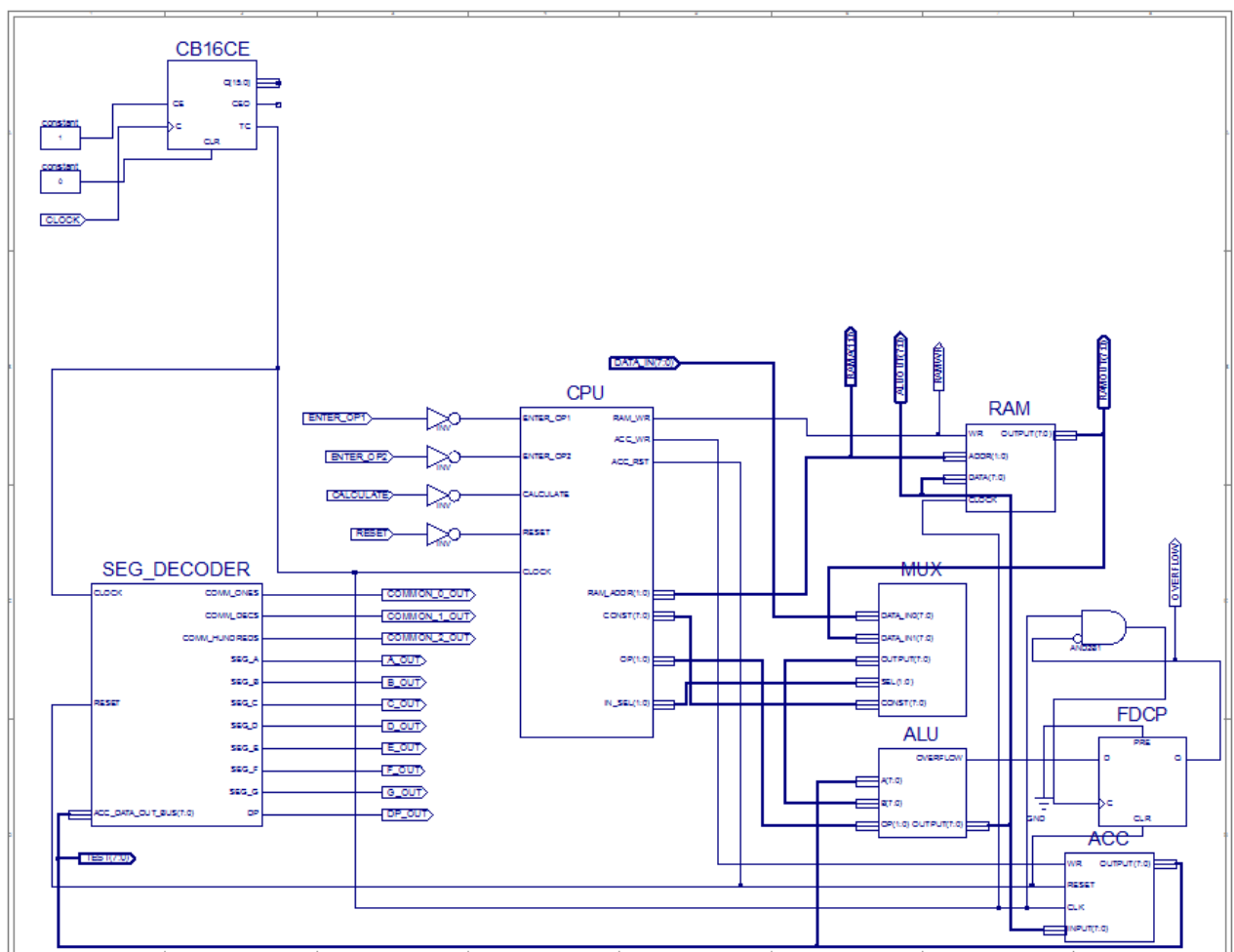


Рис.1 – Top Level

Файл ACC.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity ACC is
```

```

Port ( WR : in STD_LOGIC;
      RESET : in STD_LOGIC;
      CLK : in STD_LOGIC;
      INPUT : in STD_LOGIC_VECTOR (7 downto 0);
      OUTPUT : out STD_LOGIC_VECTOR (7 downto 0));
end ACC;

```

architecture ACC_arch of ACC is

```

    signal DATA : STD_LOGIC_VECTOR (7 downto 0);
begin
    process (CLK)
    begin
        if rising_edge(CLK) then
            if RESET = '1' then
                DATA <= (others => '0');
            elsif WR = '1' then
                DATA <= INPUT;
            end if;
        end if;
    end process;

```

```

    OUTPUT <= DATA;

```

```

end ACC_arch;

```

Файл ALU.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

entity ALU is

```
Port ( A : in  STD_LOGIC_VECTOR(7 downto 0);
      B : in  STD_LOGIC_VECTOR(7 downto 0);
      OP : in  STD_LOGIC_VECTOR(1 downto 0);
      OUTPUT : out STD_LOGIC_VECTOR(7 downto 0);
      OVERFLOW: out STD_LOGIC);
```

end ALU;

architecture ALU_Behavioral of ALU is

```
    signal ALUR: STD_LOGIC_VECTOR(15 downto 0) := (others => '0');
    signal Carry: STD_LOGIC := '0';
begin
    process(A, B, OP)
    begin
        case (OP) is
            when "01" => ALUR <= ("00000000" & A) + ("00000000" & B);
            when "10" => ALUR <=
std_logic_vector(to_unsigned((to_integer(unsigned(("00000000" & A))) *
to_integer(unsigned(("00000000" & B)))),16));
            when "11" => ALUR <= std_logic_vector(unsigned(("00000000" & A)) sll
to_integer(unsigned(B))) and x"00FF";
            when others => ALUR <= ("00000000" & B);
        end case;
    end process;
    OUTPUT <= ALUR(7 downto 0);
    OVERFLOW <= ALUR(8) OR ALUR(9) OR ALUR(10) OR ALUR(11) OR ALUR(12)
OR ALUR(13) OR ALUR(14) OR ALUR(15);
end ALU_Behavioral;
```

Файл MUX.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

entity MUX is

```
    PORT(  
        SEL: in STD_LOGIC_VECTOR(1 downto 0);  
        CONST: in STD_LOGIC_VECTOR(7 downto 0);  
        --CONST1: in STD_LOGIC_VECTOR()  
        DATA_IN0: in STD_LOGIC_VECTOR(7 downto 0);  
        DATA_IN1: in STD_LOGIC_VECTOR(7 downto 0);  
        OUTPUT: out STD_LOGIC_VECTOR(7 downto 0)  
    );
```

end MUX;

architecture Behavioral of MUX is

begin

```
    process (SEL, DATA_IN0, DATA_IN1, CONST)  
    begin  
        if (SEL = "00") then  
            OUTPUT <= DATA_IN0;  
        elsif (SEL = "01") then  
            OUTPUT <= DATA_IN1;  
        else  
            OUTPUT <= CONST;  
        end if;  
    end process;
```

end Behavioral;

Файл RAM.vhd

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.NUMERIC_STD.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

entity RAM is

port(

WR : IN STD_LOGIC;

ADDR : IN STD_LOGIC_VECTOR(1 DOWNTO 0);

DATA : IN STD_LOGIC_VECTOR(7 DOWNTO 0);

CLOCK: IN STD_LOGIC;

OUTPUT : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)

);

end RAM;

architecture RAM_arch of RAM is

type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7 downto 0);

signal UNIT : ram_type;

begin

process(ADDR, CLOCK, UNIT)

begin

if(rising_edge(CLOCK)) then

if (WR = '1') then

UNIT(conv_integer(ADDR)) <= DATA;

end if;

end if;

OUTPUT <= UNIT(conv_integer(ADDR));

end process;

end RAM_arch;

Файл SEG_DECODER.vhd

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity SEG_DECODER is

```
    port( CLOCK : IN STD_LOGIC;

          RESET : IN STD_LOGIC;

          ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7 DOWNTO 0);

          COMM_ONES          : OUT STD_LOGIC;

          COMM_DECS          : OUT STD_LOGIC;

          COMM_HUNDREDS     : OUT STD_LOGIC;

          SEG_A      : OUT STD_LOGIC;

          SEG_B      : OUT STD_LOGIC;

          SEG_C      : OUT STD_LOGIC;

          SEG_D      : OUT STD_LOGIC;

          SEG_E      : OUT STD_LOGIC;

          SEG_F : OUT STD_LOGIC;

          SEG_G      : OUT STD_LOGIC;

          DP          : OUT STD_LOGIC);
```

end SEG_DECODER;

architecture Behavioral of SEG_DECODER is

```
    signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";

    signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";

    signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
```

begin

```
    BIN_TO_BCD : process (ACC_DATA_OUT_BUS)

        variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;

        variable bcd     : STD_LOGIC_VECTOR(11 downto 0) ;
```

begin

```
    bcd      := (others => '0') ;

    hex_src   := ACC_DATA_OUT_BUS;
```

```
    for i in hex_src'range loop
```

```
        if bcd(3 downto 0) > "0100" then
```

```

        bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
    end if ;
    if bcd(7 downto 4) > "0100" then
        bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
    end if ;
    if bcd(11 downto 8) > "0100" then
        bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
    end if ;

    bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1 new entry
    hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; -- shift src + pad with 0
end loop ;

HONDREDS_BUS    <= bcd (11 downto 8);
DECS_BUS        <= bcd (7 downto 4);
ONES_BUS        <= bcd (3 downto 0);

end process BIN_TO_BCD;

```

```

INDICATE : process(CLOCK)

```

```

    type DIGIT_TYPE is (ONES, DECS, HUNDREDS);

```

```

    variable CUR_DIGIT    : DIGIT_TYPE := ONES;

```

```

    variable DIGIT_VAL      : STD_LOGIC_VECTOR(3 downto 0) := "0000";

```

```

    variable DIGIT_CTRL     : STD_LOGIC_VECTOR(6 downto 0) := "0000000";

```

```

    variable COMMONS_CTRL  : STD_LOGIC_VECTOR(2 downto 0) := "000";

```

```

    begin

```

```

        if (rising_edge(CLOCK)) then

```

```

            if(RESET = '0') then

```

```

                case CUR_DIGIT is

```

```

                    when ONES =>

```

```

                        DIGIT_VAL := ONES_BUS;

```



```

        CUR_DIGIT := DECS;
        COMMONS_CTRL := "001";
    when DECS =>
        DIGIT_VAL := DECS_BUS;
        CUR_DIGIT := HUNDREDS;
        COMMONS_CTRL := "010";
    when HUNDREDS =>
        DIGIT_VAL := HONDREDS_BUS;
        CUR_DIGIT := ONES;
        COMMONS_CTRL := "100";
    when others =>
        DIGIT_VAL := ONES_BUS;
        CUR_DIGIT := ONES;
        COMMONS_CTRL := "000";
end case;

case DIGIT_VAL is          --abcdefg
    when "0000" => DIGIT_CTRL := "1111110";
    when "0001" => DIGIT_CTRL := "0110000";
    when "0010" => DIGIT_CTRL := "1101101";
    when "0011" => DIGIT_CTRL := "1111001";
    when "0100" => DIGIT_CTRL := "0110011";
    when "0101" => DIGIT_CTRL := "1011011";
    when "0110" => DIGIT_CTRL := "1011111";
    when "0111" => DIGIT_CTRL := "1110000";
    when "1000" => DIGIT_CTRL := "1111111";
    when "1001" => DIGIT_CTRL := "1111011";
    when others => DIGIT_CTRL := "0000000";
end case;

else
    DIGIT_VAL := ONES_BUS;
    CUR_DIGIT := ONES;
    COMMONS_CTRL := "000";

```

end if;

COMM_ONES <= not COMMONS_CTRL(0);

COMM_DECS <= not COMMONS_CTRL(1);

COMM_HUNDREDS <= not COMMONS_CTRL(2);

SEG_A <= not DIGIT_CTRL(6);

SEG_B <= not DIGIT_CTRL(5);

SEG_C <= not DIGIT_CTRL(4);

SEG_D <= not DIGIT_CTRL(3);

SEG_E <= not DIGIT_CTRL(2);

SEG_F <= not DIGIT_CTRL(1);

SEG_G <= not DIGIT_CTRL(0);

DP <= '1';

end if;

end process INDICATE;

end Behavioral;

Файл CPU.vhd

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity CPU is

port(ENTER_OP1 : IN STD_LOGIC;

ENTER_OP2 : IN STD_LOGIC;

CALCULATE : IN STD_LOGIC;

RESET : IN STD_LOGIC;

CLOCK : IN STD_LOGIC;

RAM_WR : OUT STD_LOGIC;

RAM_ADDR : OUT STD_LOGIC_VECTOR(1 DOWNTO 0);

```

CONST : OUT STD_LOGIC_VECTOR(7 DOWNT0 0);
ACC_WR : OUT STD_LOGIC;
ACC_RST : OUT STD_LOGIC;
IN_SEL : OUT STD_LOGIC_VECTOR(1 downto 0);
OP : OUT STD_LOGIC_VECTOR(1 DOWNT0 0));

end CPU;

architecture CPU_arch of CPU is

type STATE_TYPE is (RST, IDLE, LOAD_OP1, LOAD_OP2, RUN_CALC0, RUN_CALC1,
RUN_CALC2, RUN_CALC3, RUN_CALC4, FINISH);

signal CUR_STATE : STATE_TYPE;
signal NEXT_STATE : STATE_TYPE;

begin

    SYNC_PROC: process (CLOCK)
    begin
        if (rising_edge(CLOCK)) then
            if (RESET = '1') then
                CUR_STATE <= RST;
            else
                CUR_STATE <= NEXT_STATE;
            end if;
        end if;
    end process;

    NEXT_STATE_DECODE: process (CLOCK, ENTER_OP1, ENTER_OP2, CALCULATE)
    begin
        NEXT_STATE <= CUR_STATE;

        case(CUR_STATE) is
            when RST =>

```

```

        NEXT_STATE <= IDLE;
    when IDLE =>
        if (ENTER_OP1 = '1') then
            NEXT_STATE <= LOAD_OP1;
        elsif (ENTER_OP2 = '1') then
            NEXT_STATE <= LOAD_OP2;
        elsif (CALCULATE = '1') then
            NEXT_STATE <= RUN_CALC0;
        else
            NEXT_STATE <= IDLE;
        end if;
    when LOAD_OP1 =>
        NEXT_STATE <= IDLE;
    when LOAD_OP2 =>
        NEXT_STATE <= IDLE;
    when RUN_CALC0 =>
        NEXT_STATE <= RUN_CALC1;
    when RUN_CALC1 =>
        NEXT_STATE <= RUN_CALC2;
    when RUN_CALC2 =>
        NEXT_STATE <= RUN_CALC3;
    when RUN_CALC3 =>
        NEXT_STATE <= RUN_CALC4;
    when RUN_CALC4 =>
        NEXT_STATE <= FINISH;
    when FINISH =>
        NEXT_STATE <= FINISH;
    when others =>
        NEXT_STATE <= IDLE;
end case;
end process;

```

OUTPUT_DECODE: process (CUR_STATE)

begin

case (CUR_STATE) is

when RST =>

RAM_WR <= '0';

RAM_ADDR <= "00";

CONST <= "00000000";

ACC_WR <= '0';

ACC_RST <= '1';

IN_SEL <= "00";

OP <= "00";

when LOAD_OP1 =>

RAM_WR <= '1';

RAM_ADDR <= "00";

CONST <= "00000000";

ACC_WR <= '0';

ACC_RST <= '1';

IN_SEL <= "00";

OP <= "00";

when LOAD_OP2 =>

RAM_WR <= '1';

RAM_ADDR <= "01";

CONST <= "00000000";

ACC_WR <= '0';

ACC_RST <= '1';

IN_SEL <= "00";

OP <= "00";

when RUN_CALC0 =>

RAM_WR <= '0';

RAM_ADDR <= "00";

CONST <= "00000000";

ACC_WR <= '1';

ACC_RST <= '0';

IN_SEL <= "01";

```

        OP <= "00";
when RUN_CALC1 =>
    RAM_WR <= '0';
    RAM_ADDR <= "01";
    CONST <= "00000000";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "01";
    OP <= "01";
when RUN_CALC2 =>
    RAM_WR <= '0';
    RAM_ADDR <= "01";
    CONST <= "00001010";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "10";
    OP <= "01";
when RUN_CALC3 =>
    RAM_WR <= '0';
    RAM_ADDR <= "01";
    CONST <= "00000010";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "10";
    OP <= "10";
when RUN_CALC4 =>
    RAM_WR <= '0';
    RAM_ADDR <= "01";
    CONST <= "00000000";
    ACC_WR <= '1';
    ACC_RST <= '0';
    IN_SEL <= "01";
    OP <= "11";

```

when IDLE =>

```
RAM_WR <= '0';  
RAM_ADDR <= "00";  
CONST <= "00000000";  
ACC_WR <= '0';  
ACC_RST <= '0';  
IN_SEL <= "00";  
OP <= "00";
```

when others =>

```
RAM_WR <= '0';  
RAM_ADDR <= "00";  
CONST <= "00000000";  
ACC_WR <= '0';  
ACC_RST <= '0';  
IN_SEL <= "00";  
OP <= "00";
```

end case;

end process;

end CPU_arch;

Часові діаграми:

 


Рис. 2 – Часова діаграма ACC

 


Рис. 3 – Часова діаграма ALU

 


Рис. 4 – Часова діаграма MUX

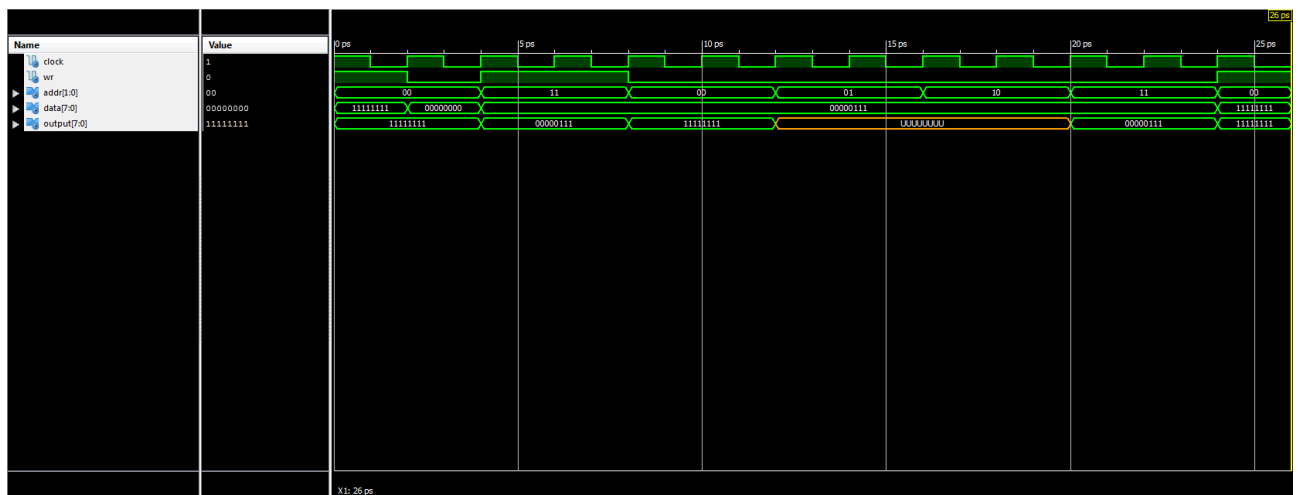


Рис. 5 – Часова діаграма RAM

 


Рис. 6 – Часова діаграма SEG_DECODER

 


Рис. 7 – Часова діаграма TopLevel

Файл TopLevelTest.vhd

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.numeric_std.ALL;

LIBRARY UNISIM;

USE UNISIM.Vcomponents.ALL;

ENTITY TopLevel_TopLevel_sch_tb IS

END TopLevel_TopLevel_sch_tb;

ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS

    COMPONENT TopLevel

    PORT( CLOCK      :    IN    STD_LOGIC;

          RESET      :    IN    STD_LOGIC;

          ENTER_OP1   :    IN    STD_LOGIC;

          ENTER_OP2   :    IN    STD_LOGIC;

          CALCULATE   :    IN    STD_LOGIC;

          DATA_IN    :    IN    STD_LOGIC_VECTOR (7 DOWNT0 0);

          COMMON_0_OUT :    OUT   STD_LOGIC;

          COMMON_1_OUT :    OUT   STD_LOGIC;

          COMMON_2_OUT :    OUT   STD_LOGIC;

          TEST: OUT STD_LOGIC_VECTOR(7 downto 0);

          A_OUT:      OUT   STD_LOGIC;

    
```

```

    B_OUT:      OUT  STD_LOGIC;
    C_OUT:      OUT  STD_LOGIC;
    D_OUT:      OUT  STD_LOGIC;
    E_OUT:      OUT  STD_LOGIC;
    F_OUT:      OUT  STD_LOGIC;
    G_OUT:      OUT  STD_LOGIC;
    DP_OUT      :      OUT  STD_LOGIC;

    RAMOUT: OUT STD_LOGIC_VECTOR(7 downto 0);
    ALUOUT: OUT STD_LOGIC_VECTOR(7 downto 0);
    RAMA: OUT STD_LOGIC_VECTOR(1 downto 0);
    RAMWR: OUT STD_LOGIC;

    OVERFLOW  :      OUT  STD_LOGIC);
END COMPONENT;

SIGNAL CLOCK  :      STD_LOGIC := '0';
SIGNAL RESET  :      STD_LOGIC;
SIGNAL ENTER_OP1  :      STD_LOGIC;
SIGNAL ENTER_OP2  :      STD_LOGIC;
SIGNAL CALCULATE  :      STD_LOGIC;
SIGNAL DATA_IN    :      STD_LOGIC_VECTOR (7 DOWNT0 0);
SIGNAL COMMON_0_OUT  :      STD_LOGIC;
SIGNAL COMMON_1_OUT  :      STD_LOGIC;
SIGNAL COMMON_2_OUT  :      STD_LOGIC;
SIGNAL A_OUT  :      STD_LOGIC;
SIGNAL B_OUT  :      STD_LOGIC;
SIGNAL C_OUT  :      STD_LOGIC;
SIGNAL D_OUT  :      STD_LOGIC;
SIGNAL E_OUT  :      STD_LOGIC;
SIGNAL F_OUT  :      STD_LOGIC;
SIGNAL G_OUT  :      STD_LOGIC;
SIGNAL DP_OUT :      STD_LOGIC;
SIGNAL OVERFLOW  :      STD_LOGIC;

    SIGNAL TEST: STD_LOGIC_VECTOR(7 downto 0);

```

```
SIGNAL TEST2: STD_LOGIC_VECTOR(7 downto 0);  
signal RAMOUT: STD_LOGIC_VECTOR(7 downto 0);  
signal ALUOUT: STD_LOGIC_VECTOR(7 downto 0);  
signal RAMA: STD_LOGIC_VECTOR(1 downto 0);  
signal RAMWR: STD_LOGIC;
```

```
constant CLKP: time := 12ms;
```

```
BEGIN
```

```
UUT: TopLevel PORT MAP(
```

```
    CLOCK => CLOCK,  
    RESET => RESET,  
    ENTER_OP1 => ENTER_OP1,  
    ENTER_OP2 => ENTER_OP2,  
    CALCULATE => CALCULATE,  
    DATA_IN => DATA_IN,  
    COMMON_0_OUT => COMMON_0_OUT,  
    COMMON_1_OUT => COMMON_1_OUT,  
    COMMON_2_OUT => COMMON_2_OUT,  
    A_OUT => A_OUT,  
    B_OUT => B_OUT,  
    C_OUT => C_OUT,  
    D_OUT => D_OUT,  
    E_OUT => E_OUT,  
    F_OUT => F_OUT,  
    G_OUT => G_OUT,  
    DP_OUT => DP_OUT,  
    OVERFLOW => OVERFLOW,  
    TEST => TEST,  
    RAMOUT => RAMOUT,  
    ALUOUT => ALUOUT,
```

```
        RAMA => RAMA,  
        RAMWR => RAMWR  
    );
```

```
    CLOCK_process: process  
begin  
    CLOCK <= '0';  
    wait for 83ns;  
    CLOCK <= '1';  
    wait for 83ns;  
end process;
```

```
tb : PROCESS  
BEGIN
```

```
    lp1: for i in 1 to 1 loop  
        lp2: for j in 2 to 2 loop  
            TEST2 <= std_logic_vector(to_unsigned((i + j + 10) * 2, 8) sll j);  
            ENTER_OP1 <= '1';  
            ENTER_OP2 <= '1';  
            CALCULATE <= '1';  
            DATA_IN <= (others => '0');  
            RESET <= '0';  
            wait for CLKP;  
            RESET <= '1';  
            wait for CLKP;  
            DATA_IN <= std_logic_vector(to_unsigned(i, 8));  
            ENTER_OP1 <= '0';  
            wait for CLKP;  
            ENTER_OP1 <= '1';  
            wait for CLKP;  
            DATA_IN <= std_logic_vector(to_unsigned(j, 8));  
            ENTER_OP2 <= '0';
```

```

        wait for CLKP;
        ENTER_OP2 <= '1';
        wait for CLKP;
        CALCULATE <= '0';
        wait for CLKP* 7;
        assert TEST = TEST2 severity FAILURE;
        wait for CLKP;

    end loop;

end loop;

WAIT;
END PROCESS;

END;
```

 


Рис.8 – 7-сегментний індикатор

Переглянемо часову діаграму 7seg decoder.

Бачимо, що для вхідного числа $0110\ 1000\ (2) = 104(10)$

Ми отримуємо такі значення(якщо значення не вказане, вважаємо його за одиницю):

COMM_ONES = 0: F, G, B, C = 0, що відповідає числу 4

COMM_DECS = 0: A, B, C, D, E, F = 0, що відповідає числу 0

COMM_HUNDREDS = 0: B, C = 0, що відповідає числу 1

Отримуємо значення 104, що збігається з даним йому.

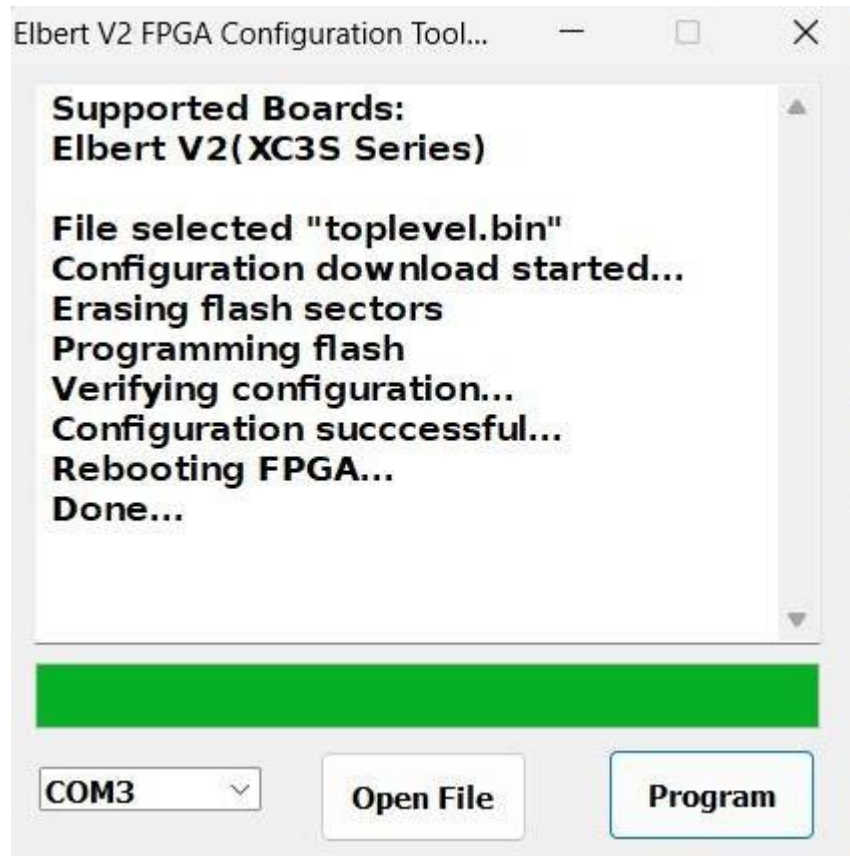


Рис.9 – Успішна прошивка

Висновок: Виконуючи дану лабораторну роботу я навчився реалізовувати цифровий автомат для обчислення значення виразів використовуючи засоби VHDL.